

Digital System Design

Design of Mealy and Moore Finite State Machines

Alfonso Fernandez

Academia de Sistemas Digitales
Escuela Superior de Cómputo, ESCOM
Instituto Politécnico Nacional, IPN

Introduction

Design Examples of Mealy FSM

Design Examples of Moore FSM

Introduction

Design Examples of Mealy FSM

Design Examples of Moore FSM

Finite Automata


Finite automata are abstract computing devices or **machines**, which are useful model for important hardware and software applications.

Finite automata are composed by discrete inputs, outputs, states and set of transitions, which depend on input symbols, from state to state. They are defined by the 5-tuples $M = (Q, \Sigma, \delta, q_0, F)$, where

- Q is a finite state set
- Σ is a finite alphabet set
- $\delta: Q \times \Sigma \rightarrow Q$ is the transition function
- $q_0 \in Q$ is the initial state
- $F \subset Q$ is the set of accepted states


Mealy Machines

 - Next state depends on present state and inputs
- Output is a function of present state and inputs



Moore Machines

 - Next state depends on present state and inputs
- Output is a function of present state




- From the State Diagram, obtain the State Table and Transition Table.
- Construct the Karnaugh maps using the Transition Table.
- Select the flip-flop to be used in the design.
- Using the Karnaugh maps derive the optimum input equations for the selected flip-flops.

Introduction

Design Examples of Mealy FSM

Design Examples of Moore FSM

Example 1: Serial Adder

 

State Table and Transition Table

Present State	Inputs		Next State	Output	Transition
A	x	y	A_+	z	f_A
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	α
1	0	0	0	1	β
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	1

Design with JK Flip-Flops

f_A		$x y$			
		00	01	11	10
A	0	0	0	α	0
	1	β	1	1	1

$$J_A = x y$$


$$K_A = \overline{x} \overline{y} = \overline{x + y}$$

z


$x y$	00	01	11	10
A				
0	0	1	0	1
1	1	0	1	0

$$z = A \oplus x \oplus y$$


Circuit Diagram

 

Timing Diagram

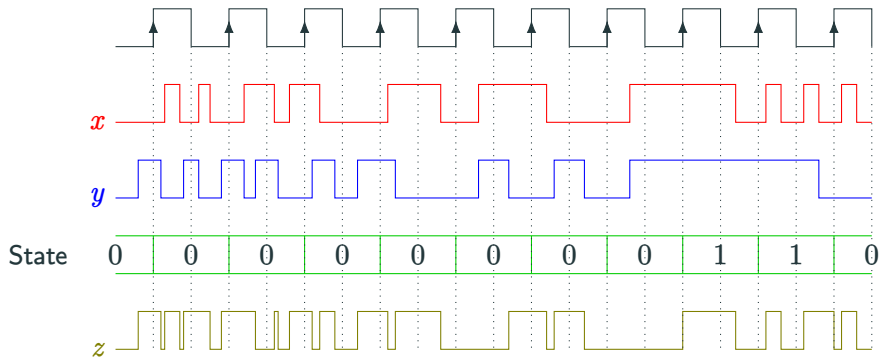

Example 2: State Diagram

 

State Table and Transition Table

Present State			Inputs		Next State			Outputs		Transitions		
A	B	C	x	y	A_+	B_+	C_+	z	w	f_A	f_B	f_C
0	0	0	0	X	0	0	0	X	X	0	0	0
0	0	0	1	X	0	0	1	X	X	0	0	α
0	0	1	X	0	0	1	0	0	1	0	α	β
0	0	1	X	1	0	0	1	1	0	0	0	1
0	1	0	X	X	1	0	0	X	X	α	β	0
1	0	0	X	0	1	0	0	1	1	1	0	0
1	0	0	X	1	1	0	1	0	0	1	0	α
1	0	1	X	0	0	0	1	1	1	β	0	1
1	0	1	X	1	0	1	0	1	0	β	α	β

Karnaugh Maps for z and w

z

$xy \backslash ABC$	000	001	011	010	110	111	101	100
00	X	0	X	X	X	X	1	1
01	X	1	X	X	X	X	1	0
11	X	1	X	X	X	X	1	0
10	X	0	X	X	X	X	1	1

$$z = yC + \bar{y}A$$

w

$xy \backslash ABC$	000	001	011	010	110	111	101	100
00	X	1	X	X	X	X	1	1
01	X	0	X	X	X	X	0	0
11	X	0	X	X	X	X	0	0
10	X	1	X	X	X	X	1	1

$$w = \bar{y}$$

Karnaugh Maps for f_A and f_B

f_A

$xy \backslash ABC$	000	001	011	010	110	111	101	100
00	0	0	X	α	X	X	β	1
01	0	0	X	α	X	X	β	1
11	0	0	X	α	X	X	β	1
10	0	0	X	α	X	X	β	1

$$J_A = B$$

$$K_A = C$$

f_B

$xy \backslash ABC$	000	001	011	010	110	111	101	100
00	0	α	X	β	X	X	0	0
01	0	0	X	β	X	X	α	0
11	0	0	X	β	X	X	α	0
10	0	α	X	β	X	X	0	0

$$J_B = (y \odot A)C$$

$$K_B = 1$$


Karnaugh Map for f_C

f_C		ABC							
xy		000	001	011	010	110	111	101	100
		0	β	X	0	X	X	1	0
00									
01		0	1	X	0	X	X	β	α
11		α	1	X	0	X	X	β	α
10		α	β	X	0	X	X	1	0


$$J_C = yA + x\overline{A}\overline{B}$$

$$K_C = y \odot A$$

Circuit Diagram

 

Timing Diagram

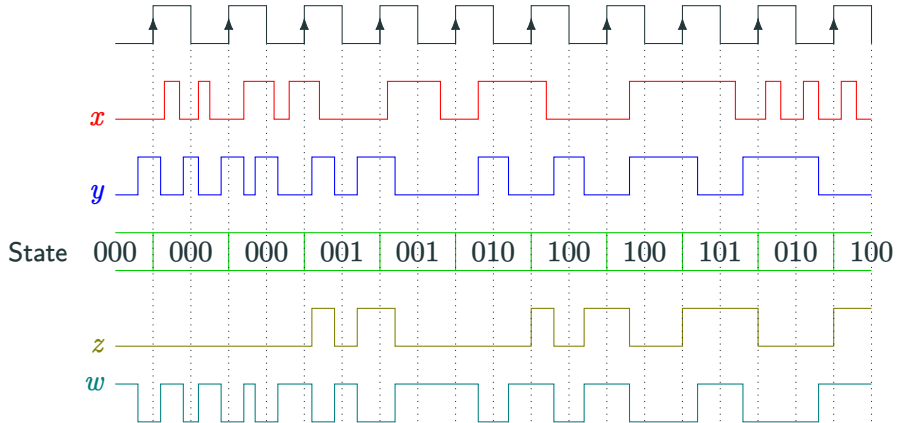


Introduction

Design Examples of Mealy FSM

Design Examples of Moore FSM

Example 1: Divisible by Three Detector

 

State Table and Transition Table

Present State		Input	Next State		Output	Transitions	
A	B		A_+	B_+		f_A	f_B
0	0	0	0	0	1	0	0
0	0	1	0	1		0	α
0	1	0	1	1	0	α	1
0	1	1	0	0		0	β
1	1	0	0	1	0	β	1
1	1	1	1	1		1	1

Design with JK Flip-Flops

Truth table for f_A (JK Flip-Flop A):

f_A	x	AB	00	01	11	10
0	0	0	0	α	β	X
1	1	0	0	0	1	X

$$J_A = B\bar{x}$$

$$K_A = \bar{x}$$

Truth table for f_B (JK Flip-Flop B):

f_B	x	AB	00	01	11	10
0	0	0	0	1	1	X
1	1	α	β	1	X	X

$$J_A = x$$


$$K_B = \bar{A}x$$

Truth table for z (Output):


z	A	B	0	1
0	0	1	1	0
1	1	X	0	0

$$z = \bar{B}$$


Circuit Diagram

 

Timing Diagram

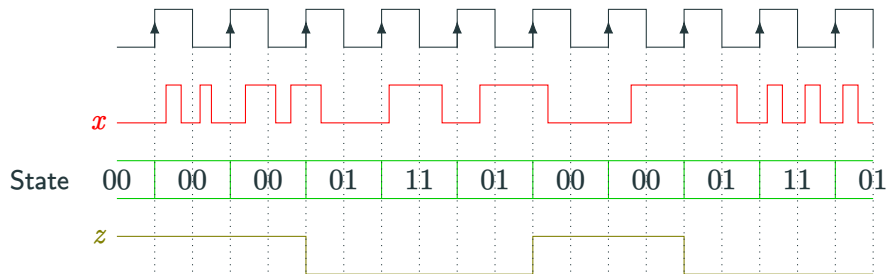

Example 2: State Diagram

 

State Table and Transition Table

Present State			Input	Next State			Output	Transitions		
A	B	C		A_+	B_+	C_+		f_A	f_B	f_C
0	0	0	0	0	0	1	1	0	0	α
0	0	0	1	0	0	0		0	0	0
0	0	1	0	0	1	1	0	0	α	1
0	0	1	1	0	0	0		0	0	β
0	1	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1		α	β	1
1	0	1	0	1	1	1	1	1	α	1
1	0	1	1	0	1	1		β	α	1
1	1	1	0	0	0	1	0	β	β	1
1	1	1	1	1	1	1		1	1	1

Design with JK Flip-Flops

f_A AB		Cx			
		00	01	11	10
X_3	00	0	0	0	0
	01	X	X	α	0
	11	X	X	1	β
	10	X	X	β	1

$$J_A = Bx$$

$$K_A = B \oplus x$$

f_B AB		Cx			
		00	01	11	10
X_3	00	0	0	0	α
	01	X	X	β	1
	11	X	X	1	β
	10	X	X	α	α

$$J_B = C\bar{x} + A\bar{B}$$

$$K_B = A \oplus x$$

f_C AB		Cx			
		00	01	11	10
X_3	00	α	0	β	1
	01	X	X	1	1
	11	X	X	1	1
	10	X	X	1	1


$$J_C = \bar{x}$$

$$K_C = \bar{A}\bar{B}x$$

z A		BC			
		00	01	11	10
	0	1	0	1	X
	1	X	1	0	X

$$z = \bar{C} + A \oplus B$$

Circuit Diagram

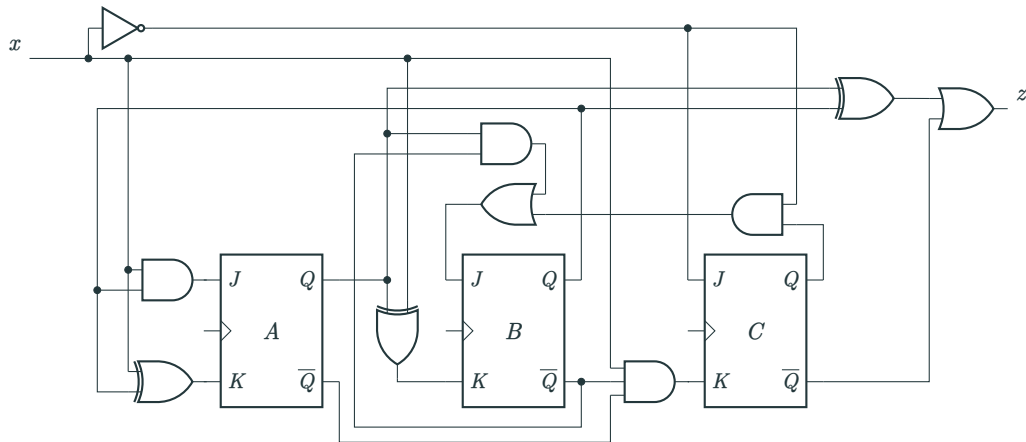

Timing Diagram

