

Digital System Design

Latches and Flip-Flops

Alfonso Fernandez

Academia de Sistemas Digitales
Escuela Superior de Cómputo, ESCOM
Instituto Politécnico Nacional, IPN

Contents

Introduction

Latches

Master-Slave Flip-Flops

Examples

Edge-Triggered Flip-Flops

Introduction

Latches

Master-Slave Flip-Flops


Examples

Edge-Triggered Flip-Flops

Combinational Systems

Combinational circuits are an interconnection of OR, AND, and NOT gates.

 
Examples of combinational systems are Encoder/Decoder, MUX/DEMUX, Adders, Multipliers, among others.




Sequential Systems

On the other side, in sequential circuits, there are two new blocks, called **latch** and **flip-flop**.

 Latches are storage elements that operate with signal levels, whereas flip-flops are controlled by a clock transition.



Latch

 

Flip-flop

Contents

Introduction

Latches


Master-Slave Flip-Flops

Examples

Edge-Triggered Flip-Flops




Simple Latch

 A simple latch can be designed using an OR gate with feedback.





Set	Q	Q_+
0	Q	Q
1	X	1

Equivalent Simple Latch

   


SR Latch (Improved Simple Latch)

  


S	R	Q_+	\overline{Q}_+
0	0	Q	\overline{Q}
0	1	0	1
1	0	1	0
1	1	0	0 (forbidden)

SR Latch with NAND Gates

 


S	R	Q_+	\overline{Q}_+
0	0	1	1 (forbidden)
0	1	1	0
1	0	0	1
1	1	Q	\overline{Q}

Critical Race

 


SR Latch with Control Input

 


En	S	R	Q_+	\overline{Q}_+
0	X	X	Q	\overline{Q}
1	0	0	Q	\overline{Q}
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1 (forbidden)

 SR Latch with Control Input: Timing Diagram




SR Latch with Control Input: Questa Simulation

 In this simulation, we consider that the propagation delay t_d in NAND gates is $0.025T$, where T is the time period of the clock signal.




 D Latch (Transparent Latch) with Control Input




En	D	Q_+	\overline{Q}_+
0	X	Q	\overline{Q}
1	0	0	1
1	1	1	0

Improved D Latch with Control Input

 


En	D	Q_+	\overline{Q}_+
0	X	Q	\overline{Q}
1	0	0	1
1	1	1	0

JK Latch with Control Input

 



En	J	K	Q_+	\overline{Q}_+
0	X	X	Q	\overline{Q}
1	0	0	Q	\overline{Q}
1	0	1	0	1
1	1	0	1	0
1	1	1	\overline{Q}	Q

T Latch with Control Input

 

En	T	Q_+	\overline{Q}_+
0	X	Q	\overline{Q}
1	0	Q	\overline{Q}
1	1	\overline{Q}	Q

Bistable Multivibrator Element

  

Introduction


Latches

Master-Slave Flip-Flops



Examples

Edge-Triggered Flip-Flops



SR Latch and Feedback

 


Stable and Unstable Feedback

  

Master-Slave SR Flip-Flop

  


Timing Diagram – Part I

 


SR Flip-flop: Characteristic Table, Characteristic Equation, and State Diagram

clk	S	R	Q_+
∇	0	0	Q
∇	0	1	0
∇	1	0	1
∇	1	1	—


 


$$Q_+ = S + \bar{R}Q$$


Timing Diagram – Part II

 

Master-Slave D Flip-Flop

  


Timing Diagram

 


D Flip-flop: Characteristic Table, Characteristic Equation, and State Diagram

clk	D	Q_+
$\neg \downarrow$	0	0
$\neg \downarrow$	1	1


$$Q_+ = D$$

 

Master-Slave JK Flip-Flop

 


Timing Diagram

 



JK Flip-flop: Characteristic Table, Characteristic Equation, and State Diagram

clk	J	K	Q_+
$\neg \text{L}$	0	0	Q
$\neg \text{L}$	0	1	0
$\neg \text{L}$	1	0	1
$\neg \text{L}$	1	1	\overline{Q}


$$Q_+ = J\overline{Q} + \overline{K}Q$$

 

Master-Slave T Flip-Flop

  


Timing Diagram

 

T Flip-flop: Characteristic Table, Characteristic Equation, and State Diagram

clk	T	Q_+
$\overline{\downarrow}$	0	Q
$\overline{\downarrow}$	1	\overline{Q}



$$Q_+ = T \oplus Q$$

 

Key Observation

Master-slave flip-flops depend on the stability of the inputs when the clock pulse is high.

  
Master-Slave JK Flip-Flop with Asynchronous Set and Clear



Characteristic Table

SET	CLR	clk	J	K	Q_+	\overline{Q}_+
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	1	1
1	1	$\overline{\text{clk}}$	0	0	Q	\overline{Q}
1	1	$\overline{\text{clk}}$	0	1	0	1
1	1	$\overline{\text{clk}}$	1	0	1	0
1	1	$\overline{\text{clk}}$	1	1	\overline{Q}	Q

 Texas Instruments: 74LS76A—Master-Slave JK Flip-Flop



Contents


Introduction


Latches


Master-Slave Flip-Flops


Examples

Edge-Triggered Flip-Flops

 

 

 

 

Introduction


Latches

Master-Slave Flip-Flops



Examples

Edge-Triggered Flip-Flops



Edge-Triggered D Flip-Flop

 

 
 
Edge-Triggered D Flip-Flop: Details ($D = 0$)



 
 
Edge-Triggered D Flip-Flop: Details ($D = 1$)



  Edge-Triggered D Flip-Flops with Asynchronous Set and Clear



Edge-Triggered JK and T Flip-Flops

  

Texas Instruments: SN7474—Edge-Triggered D Flip-Flop

